



İZMİR  
KÂTİP ÇELEBİ  
ÜNİVERSİTESİ

2010

## PROJECT

### VIBRATION DETECTION CIRCUIT

#### Students:


1-Batuhan YALÇINKAYA 160412020

2-Nurettin Uğur ALAGAŞ 160412010

**INSTRUCTOR:**Osman Akın



## **INTRODUCTION**

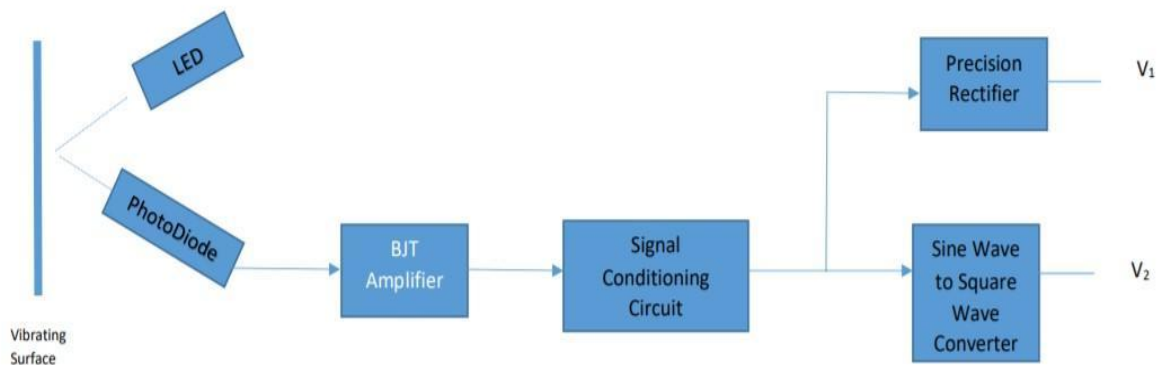

### **Aim of the Project:**

The purpose of this Project to determine the magnitude and frequency of the vibration by providing the mirror vibration and generating a signal from photodiode and expanding this signal with various circuit designs.

### **Equipment List:**

1. Blue LED
2. Mirror
3. Vibrating motor
4. Photodiode(BPW21R)
5. BJT(BC 238)
6. Opamp (LM 741)
7. Capacitors( $10\mu\text{F}$ ,  $47\mu\text{F}$ ,  $150\mu\text{F}$ )
8. Resistors

## Design Process

### 1-Photodiode and LED Design:

Photodiode is a semiconductor component that communicates with light energy. Also, it is called light-sensitive diode. The photodiode passes current from the cathode to the anode end when the light falls on it. As the light intensity falling on the photodiode increases, the reverse leakage current value increases. The photodiodes are connected reverse to the circuit.

In this project, we used BPW21R as a photo diode. Our selection of LEDs is based on the Relative Spectral Sensitivity vs Wavelength graph in Figure 1.


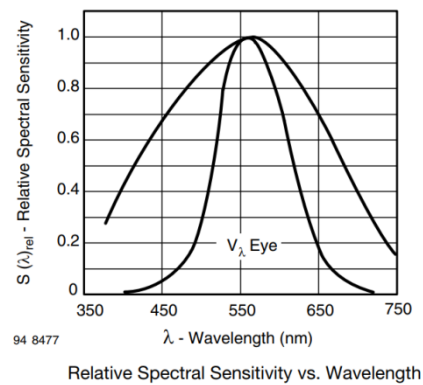



Figure-1

When choosing LED, we paid attention to the fact that the LED wavelength is between 370-700 wavelength. When we compared LED wavelengths, we decided that blue LED is the most suitable LED. Blue LED's wavelength is between 450-500.

### 2-BJT Amplifier Design

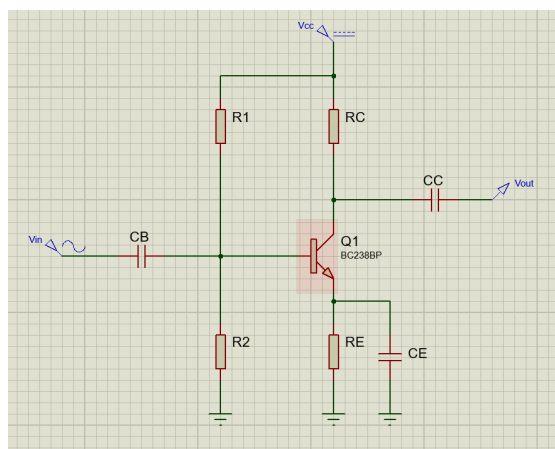

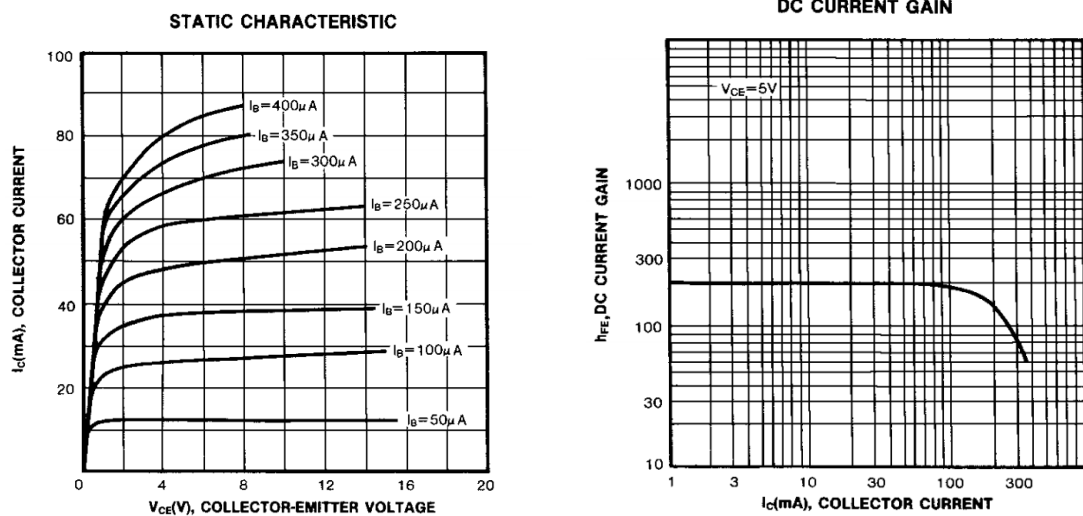In this part, we decided to design common-emitter amplifier. We preferred BC238 as BJT. When choosing the resistance values, I tried to adhere to the static characteristic graph and DC current gain in datasheet.



BJT has 3 regions which are cut-off, saturation and active region. In order to use the BJT as an amplifier, BJT must work in the active region. For this, it is important to select the resistance values properly. Otherwise, BJT can shift to saturation and cut-off regions.

The common emitter amplifiers have high voltage and current gains. It is used in the design of many devices and systems. Also, another reason for making this selection is that the common emitter amplifiers are fully stable. The characteristics of common emitter amplifiers;

- Polarization was done from a single  $V_{cc}$  source.

- Base polarization was provided with  $R_1$  and  $R_2$ .

- With the  $C_B$  capacitor, DC current was prevented from entering the input source.


- A negative feedback was provided with  $R_E$  resistance and balanced operation was provided.

- The  $C_E$  bypass capacitor is a short path for the AC signal current. This prevented the loss of AC energy on the  $R_E$  resistance. Also  $C_E$  capacitor in DC operation the stability of the transistor was preferred for providing.

- The  $R_E$  resistance reduces the gain of the transistor in AC operation. This effect of  $R_E$  was eliminated with a parallel connected  $C_E$  capacitor.

## ANALYSIS OF BJT

### -DC ANALYSIS

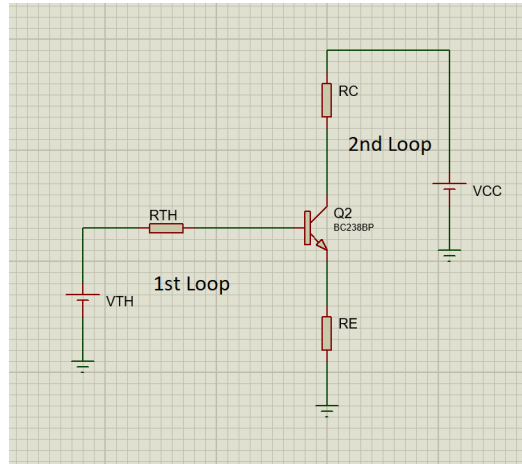

As the first step for the DC Analysis of the circuit, the DC equivalent circuit is drawn as seen above. For DC equivalent, the capacitors in the circuit are considered open circuit and the signal source is ignored. Firstly, the resistance and voltage of thevenin are calculated.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

Kirchhoff Law are applied separately for two loops.

#### 1st Loop:

$$-V_{TH} + I_B \cdot R_{TH} + V_{BE} + I_E \cdot R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$V_{TH} - V_{BE} = I_B [R_{TH} + (\beta + 1)R_E]$$


#### 2nd Loop

$$-V_{CC} + I_C \cdot R_C + V_{CE} + I_E \cdot R_E = 0$$

$$I_C = \beta I_B$$

$$V_{CC} - V_{CE} = I_B [\beta R_C + (\beta + 1)R_E]$$

## -AC ANALYSIS

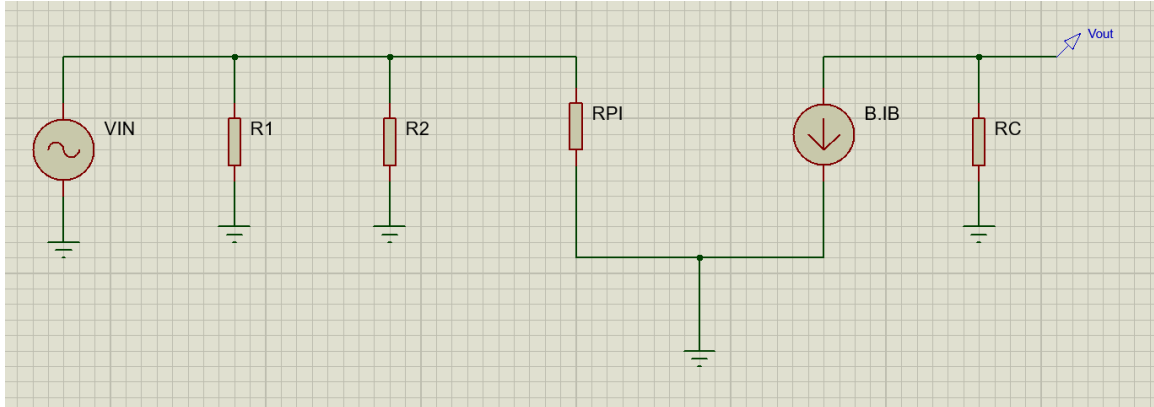

The first step for AC Analysis of the circuit is to draw the AC equivalent circuit and then apply the r- $\pi$  model as seen above. For AC equivalent, DC sources and capacitors are considered short circuit. Also, the current on the  $R_C$  is from ground to output voltage.

$$-V_{in} + i_B \cdot r_{\pi} = 0$$

$$V_{in} = i_B \cdot r_{\pi}$$

$$r_{\pi} = \frac{26mV}{I_B}$$

$$-V_{out} - \beta i_B \cdot R_C = 0$$

$$V_{out} = -\beta i_B \cdot R_C$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{\beta \cdot R_C}{r_{\pi}}$$

## DETERMINING THE RESISTORS

$$V_E = \frac{V_{CC}}{10}$$

$$R_E = \frac{V_E}{I_E} \cong \frac{V_E}{I_C}$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C}$$

$$V_{BE} = V_B - V_E \text{ so } V_B = V_{BE} + V_E$$

For the circuit to operate efficiently, it is assumed that the current through  $R_1$  and  $R_2$  should be approximately equal to and much larger than the base current (at least 10:1). This fact and the voltage-divider equation for the base voltage provide the two relationships necessary to determine the base resistors.

$$R_2 \leq \frac{1}{10} \beta R_E$$


and

$$V_{TH} = V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$
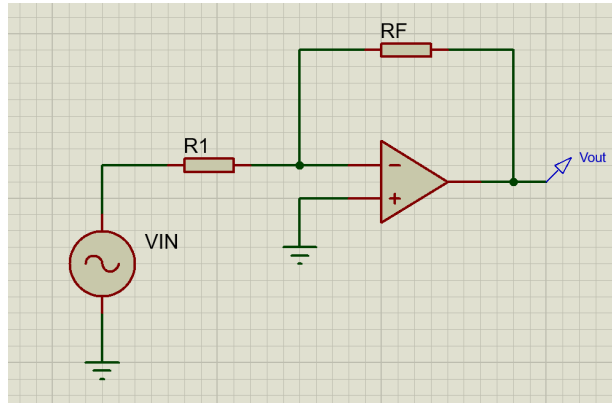
### 3-Opamp Design

Since our signal from BJT is too low, we have designed opamp. We preferred to design inverting opamp in this process.

Inverting opamp changes the phase angle of the output signal exactly 180 degrees out of phase with respect to input signal. We used two external resistors to create feedback circuit and make a closed loop circuit across the amplifier.



In the above image,  $R_1$  and  $R_F$  provide the necessary feedback throughout the opamp circuit. The  $R_1$  resistor is the signal input resistor and  $R_F$  resistor is the feedback resistor. The feedback is connected across the opamp's negative terminal and the positive terminal is connected across the ground. Also  $V_+$  and  $V_-$  is the same.

$$V_- = V_+ = 0$$

$$\frac{V_- - V_{in}}{R_1} + \frac{V_- - V_{out}}{R_F} = 0$$

$$\frac{V_{out}}{R_F} = - \frac{V_{in}}{R_1}$$




$$V_{out} = -\frac{R_F}{R_1} V_{in}$$

$$A_v = -\frac{R_F}{R_1}$$

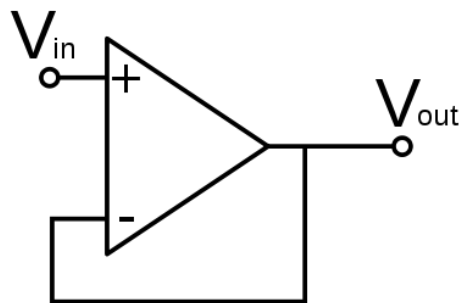
#### 4-Buffer Design

Buffer opamp circuits transmit the input signal to the output without changing it at all. We designed this circuit to make the impedances suitable and to isolate the circuits from each other. The voltage gain in the buffer circuit is 1.



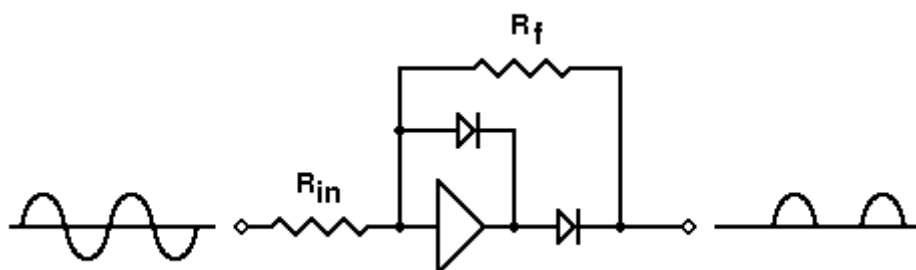
#### 5-Precision Rectifier Design

The purpose of designing this circuit was to obtain DC output. We used two 1N4001 diode. When we used diode signal converts AC to + cycle. We want to obtain DC output. So, we must to keep low ripple voltage. So, we selected high capacitor and resistor value. Signal converts nearly DC.



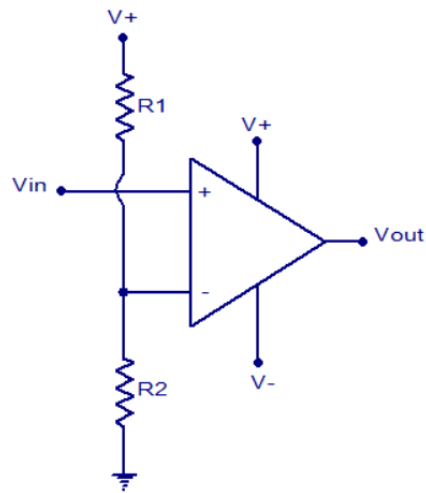
#### 6-Comparator Design

In non-inverting comparator the reference voltage was applied to the inverting input and the voltage to be compared was applied to the non-inverting input. Whenever the input voltage to be compared goes above the reference voltage, the output of the opamp swings to positive saturation and vice versa.



## CALCULATIONS, SIMULATIONS AND MEASURED

### BJT:

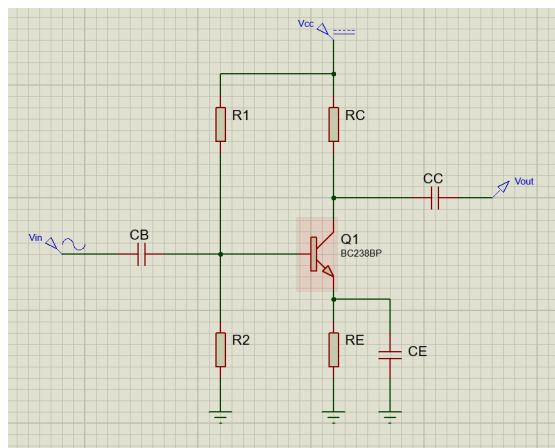

We assumed  $I_{CQ}$  and  $V_{CEQ}$  values.

$$I_{CQ} = 6mA$$

$$V_{CEQ} = 5.2V$$

$$V_{CC} = 12V$$

$$\beta = 265$$

$$V_E = \frac{1}{10} V_{CC} = \frac{1}{10} \cdot 12 = 1.2V$$

$$R_E = \frac{V_E}{I_E} \cong \frac{V_E}{I_C} = \frac{1.2}{6mA} = 200\Omega$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C} = \frac{10 - 5.2 - 1.2}{6mA} = 0.933 \approx 1k\Omega$$

$$V_B = V_{BE} + V_E = 0.7 + 1.2 = 1.9V$$

$$R_2 \leq \frac{1}{10} \beta R_E$$


$$R_2 \leq \frac{1}{10} \cdot 265 \cdot (0.2k\Omega)$$

$$R_2 = 5.3k\Omega \approx 5.1k\Omega$$


$$V_B = 1.9V = \frac{(5.2k\Omega) \cdot 12V}{R_1 + 5.2k\Omega}$$

$$1.9R_1 + 9.88 = 62.4$$

$$R_1 = 27.6k\Omega \approx 27k\Omega$$

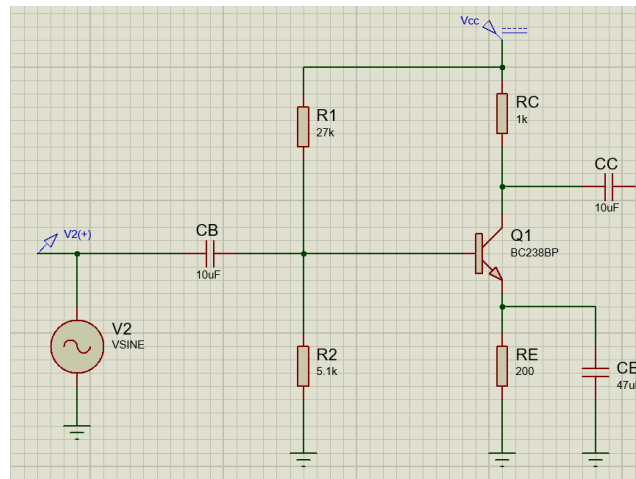

**DC Analysis:**

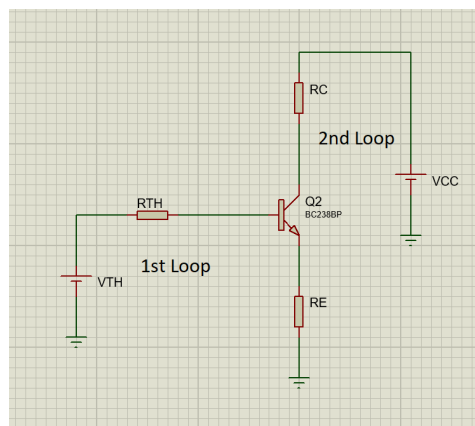

$$R_{TH} = \frac{(27k\Omega) \cdot (5.1k\Omega)}{32.1k\Omega} = 4.36k\Omega$$

$$V_{TH} = \frac{5.1k\Omega}{32.1k\Omega} 12V = 1.98V$$

$$1.98 - 0.7 = I_B(4.36k\Omega + (266)(0.2k\Omega))$$

$$I_B = 22.24\mu A$$


$$I_C = \beta I_B = 5.89mA$$

$$I_E = (\beta + 1)I_B = 5.92mA$$

$$12 - V_{CE} = (22.24 \times 10^{-6})(4360\Omega + 266 \times 200\Omega)$$

$$V_{CE} = 4.92V$$

### AC Analysis:

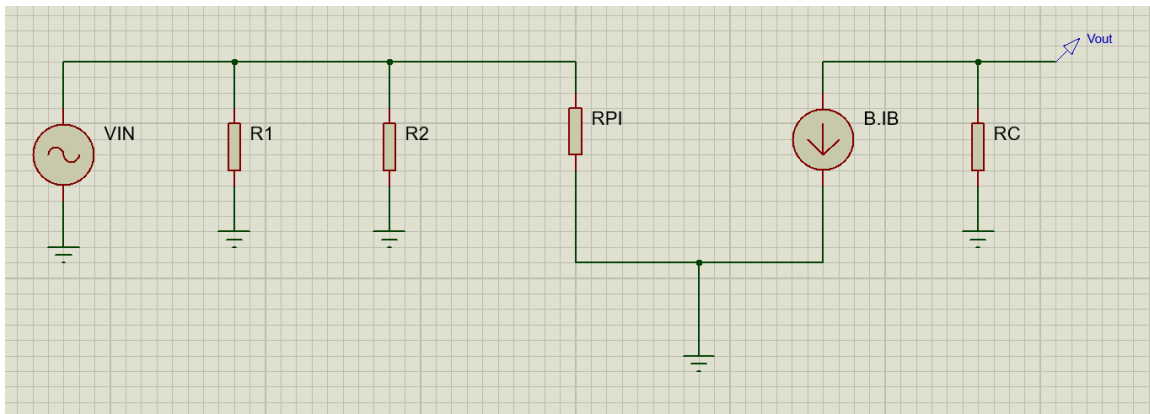

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(27k\Omega)(5.1k\Omega)}{32.1k\Omega} = 4.36k\Omega$$

$$r_\pi = \frac{26mV}{I_B} = \frac{26 \times 10^{-3}}{22.24 \times 10^{-6}} = 1.17k\Omega$$

$$V_{in} = i_b r_\pi$$

$$V_{in} = 6mV = 6 \times 10^{-3}V$$



$$i_b = \frac{6 \times 10^{-3}V}{1170\Omega} = 5.13\mu A$$

$$V_{out} = -\beta i_b R_C$$

$$V_{out} = -265(5.13 \times 10^{-6}A)(1000\Omega)$$

$$V_{out} = -1359 \times 10^{-3}V$$
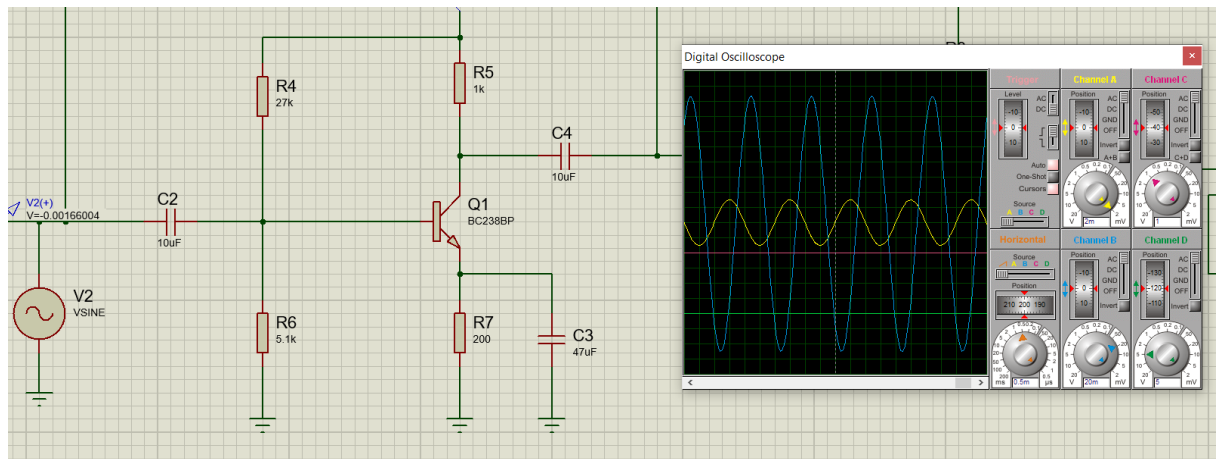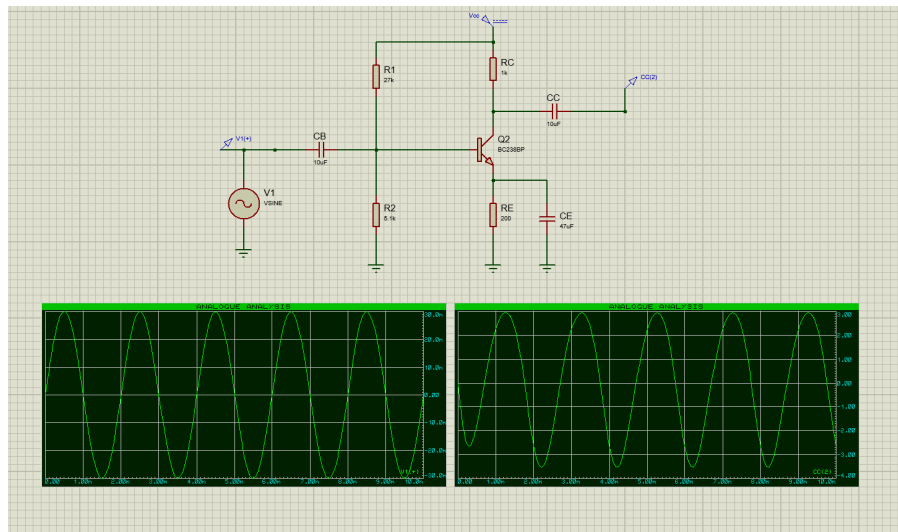
$$A_v = \frac{V_{out}}{V_{in}} = \frac{1359 \times 10^{-3}}{6 \times 10^{-3}} \approx 226$$



**OPAMP:**


$$V_{out} = -\frac{R_F}{R_1} V_{in}$$

$$A_v = -\frac{R_F}{R_1}$$


We have chosen 1k so that the resistance of  $R_1$  is almost equal to  $R_{out}$  in the BJT circuit. And then we want to have 10 gain in the opamp circuit.

$$V_{out} = -\frac{10}{1} V_{in}$$

$$A_v = -\frac{10}{1} = -10$$

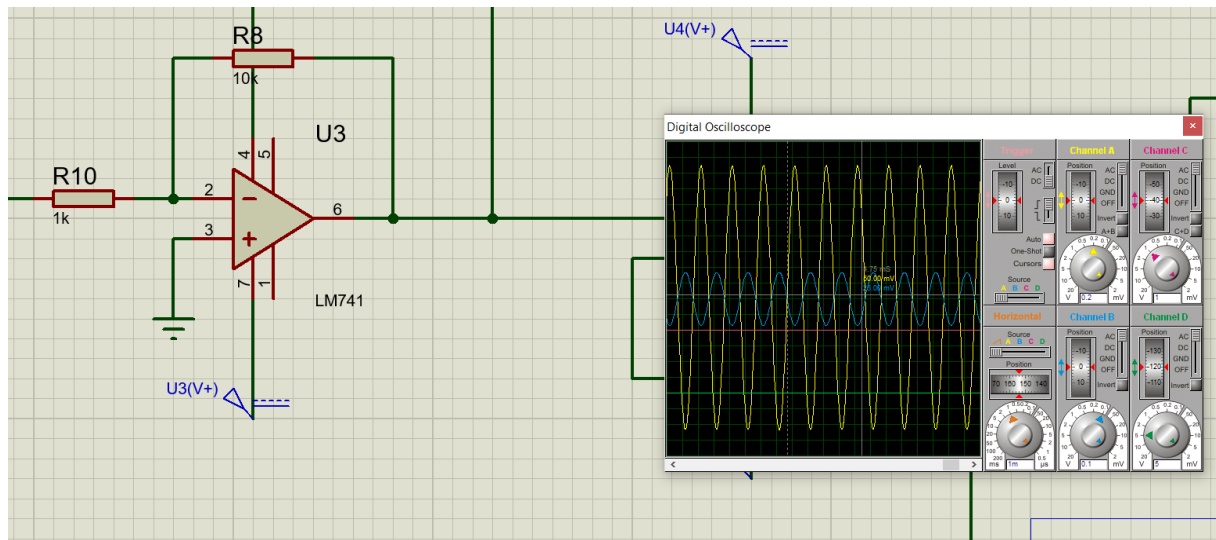


### BUFFER:

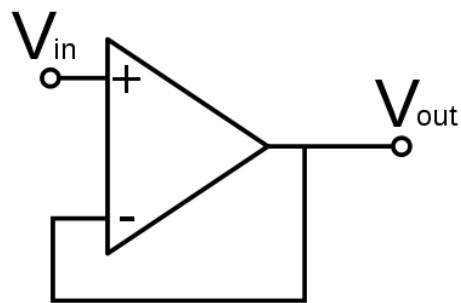

$$V_{in} = V_{out}$$

### COMPARATOR:

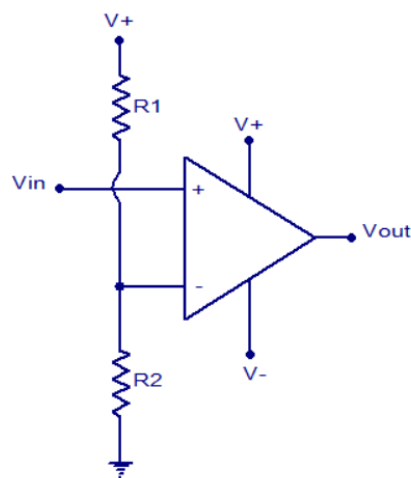


We assumed  $V_{ref}$  minimum voltage which was 0.1V to keep duty cycle at %50.

$$\frac{V_{ref}-0}{R_2} = \frac{V_+-V_{ref}}{R_1}$$

$$\frac{0.1}{R_2} = \frac{5-0.1}{R_1}$$


$$R_1 = 49R_2$$

$$R_1 = 56k \quad R_2 = 1k$$

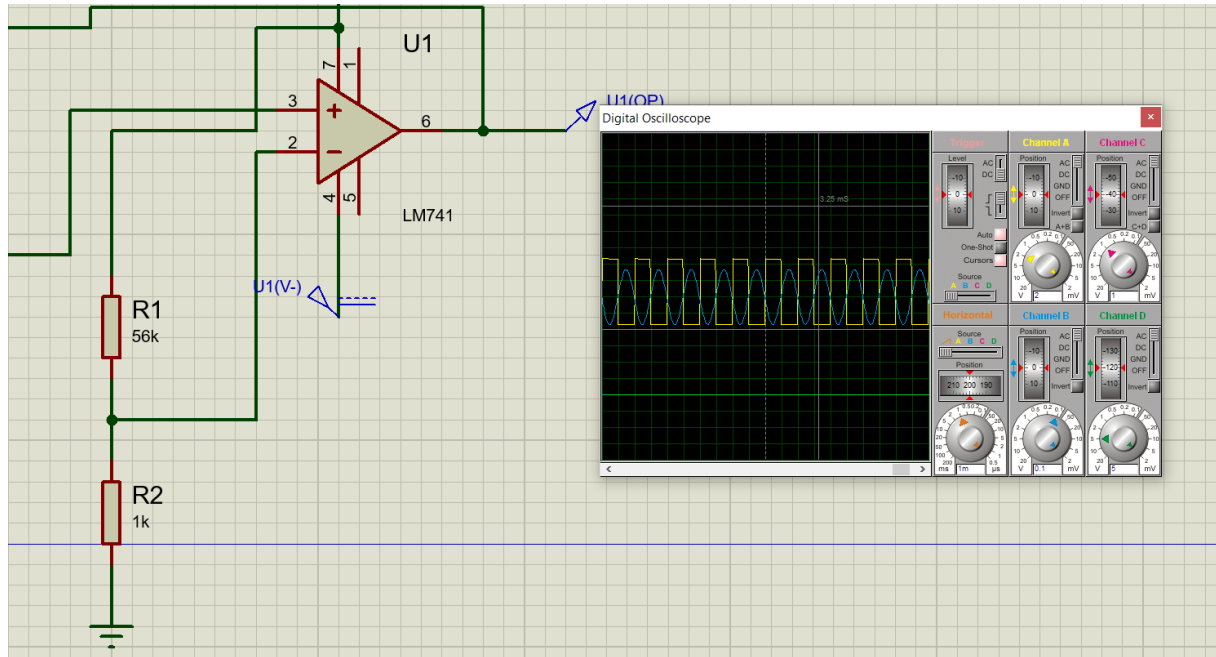


## OSCILLOSCOPE

### PHOTODIODE:

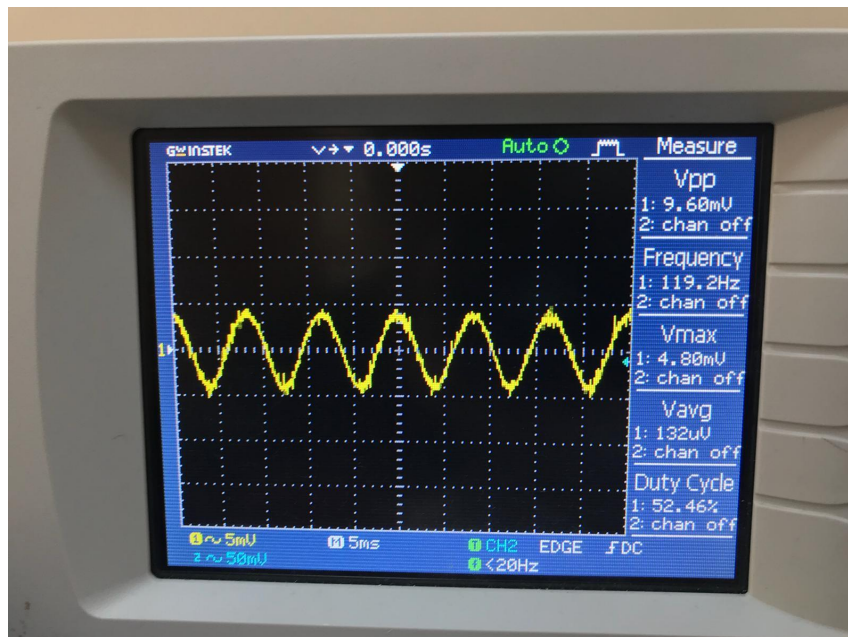


### BJT:

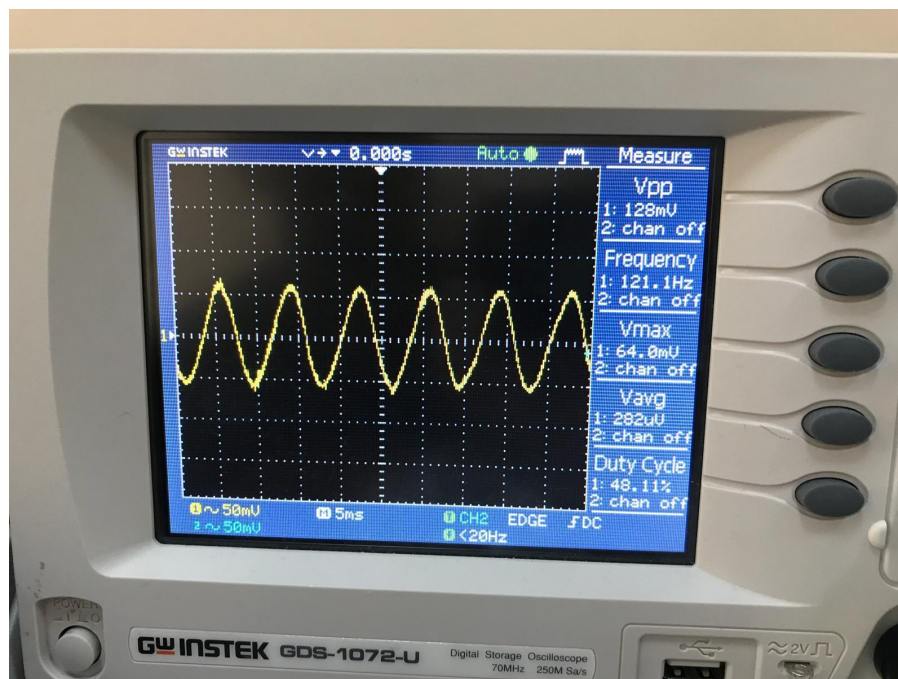





## OPAMP:

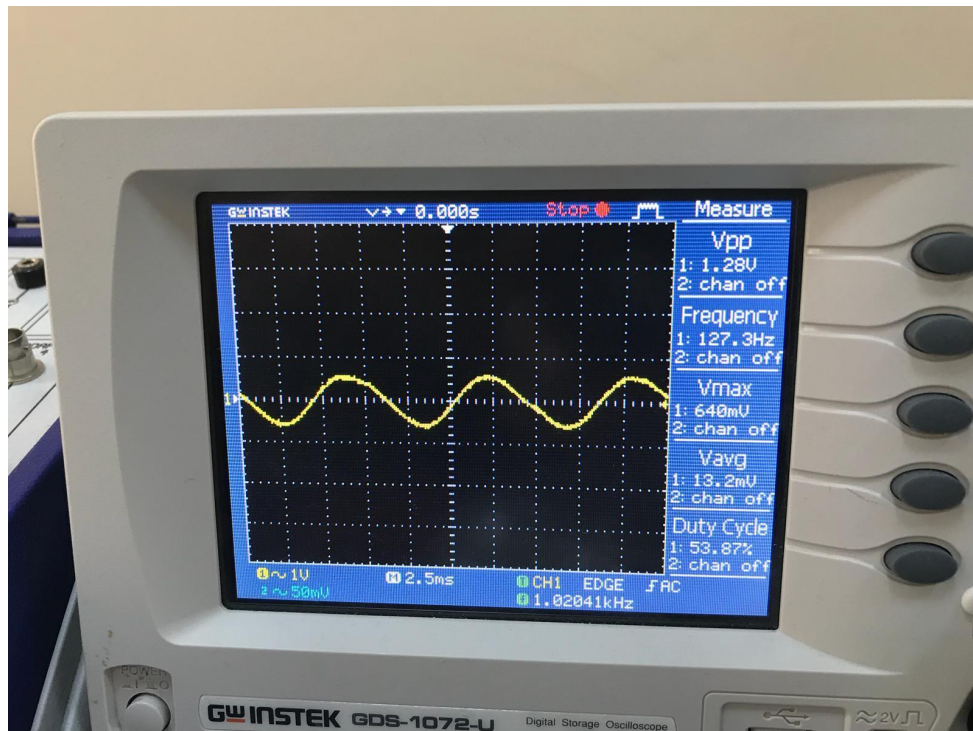


## BUFFER:

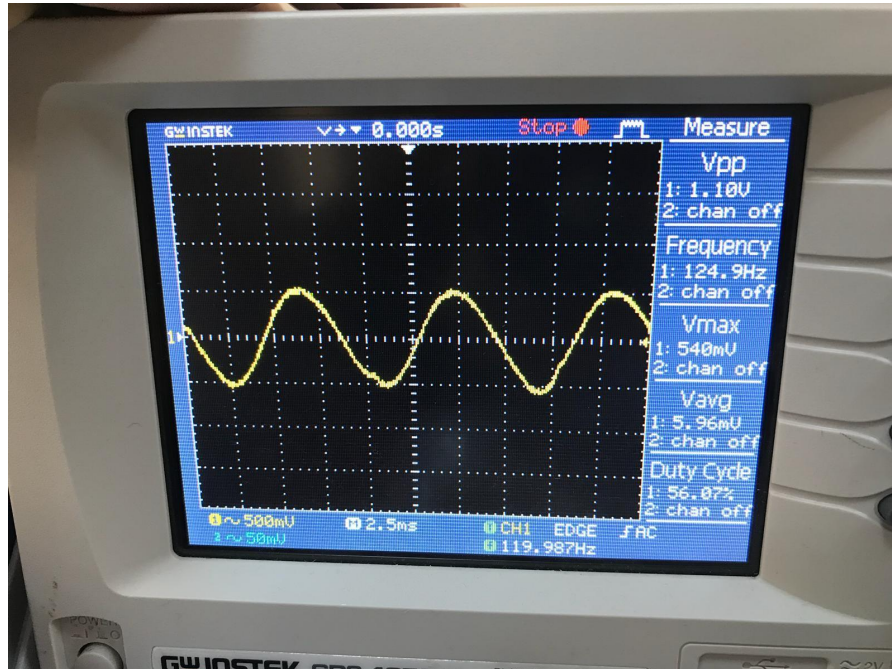

## COMPARATOR:

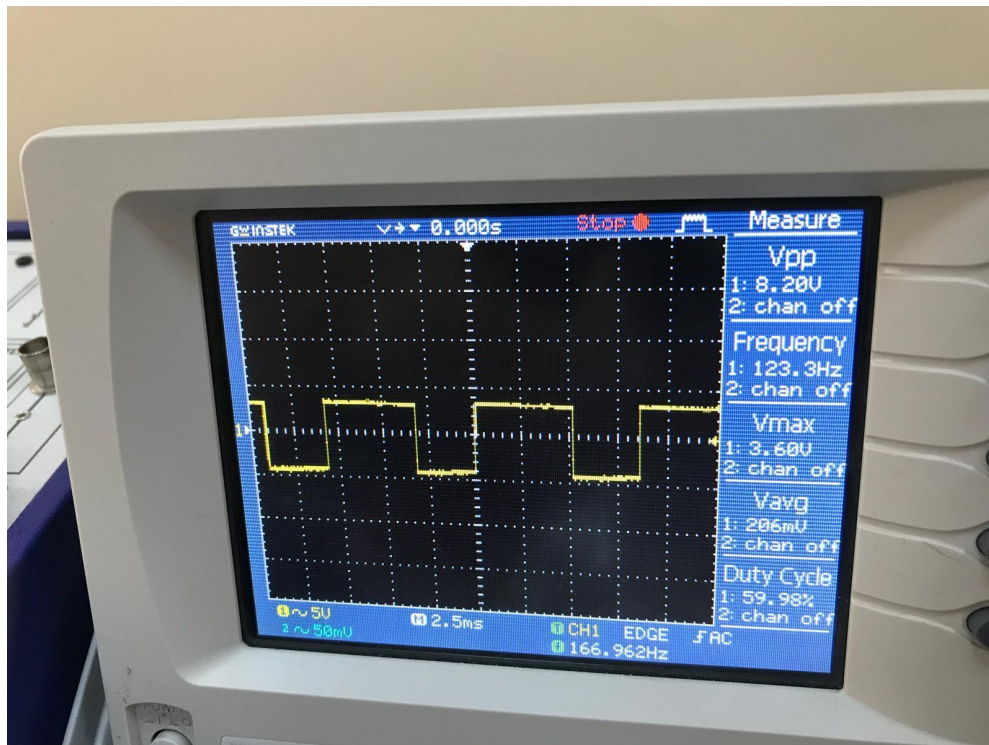

## HALF-WAVE PRECISION RECTIFIER:

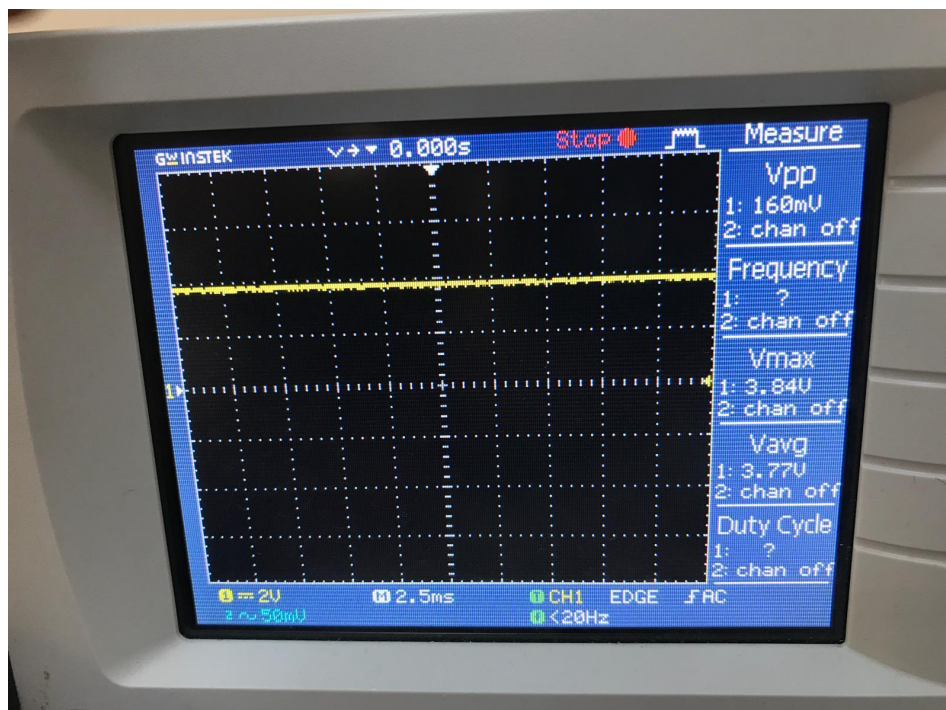

## DISCUSSION

Aim of the experiment is thanks to photodiode we have obtained voltage and current through the light from the led and filtering the signal with some special circuits and specialized the circuits for increasing current and voltage. For this we use 5 circuits. These are BJT circuit, Inverter opamp circuit, Buffer circuit, comparator and precision circuit.

Firstly we use BJT circuit. We use it as a amplifier. For this we use BC 238 transistor. For using as a amplifier we use it at active region. For this we did some special calculations. Using this calculations we assumed the resistors. At bjt in measurement our gain is -12. But it is all circuits are connected each other. If we look just BJT circuit, our gain is 100. Decreasing at gain we thought because of common ground and the output resistance is greater than the input resistance of the future circuit. If we are increasing the resistance of the input circuit of the next circuit can increase our gain

For 2. Circuit we use inverting opamp. Reason of this is the voltage which is obtained from BJT is low. At inverting opamp  $R_f/R_1$  is gain. So  $R_f > R_1$ . accordingly, we created the desired rate of gain. thanks to this we increased our voltage. But this isn't filter. For this we use buffer circuit. buffer circuit stabilizes the signal. this is preparing a nice environment for precision or comparator.

For third circuit we built comparator circuits. Aim of doing this change incoming sine wave to square wave. For this LM741 opamp. And at output we obtained 0-5 V TTL. In non-inverting comparator the reference voltage was applied to the inverting input and the voltage to be compared was applied to the non-inverting input. Whenever the input voltage to be compared goes above the reference voltage, the output of the opamp swings to positive saturation and vice versa.

Forth circuit is precision circuit. At output of this circuit 0-5 V DC voltage. At precision circuit we used diode. Diode allows current to flow in one direction.